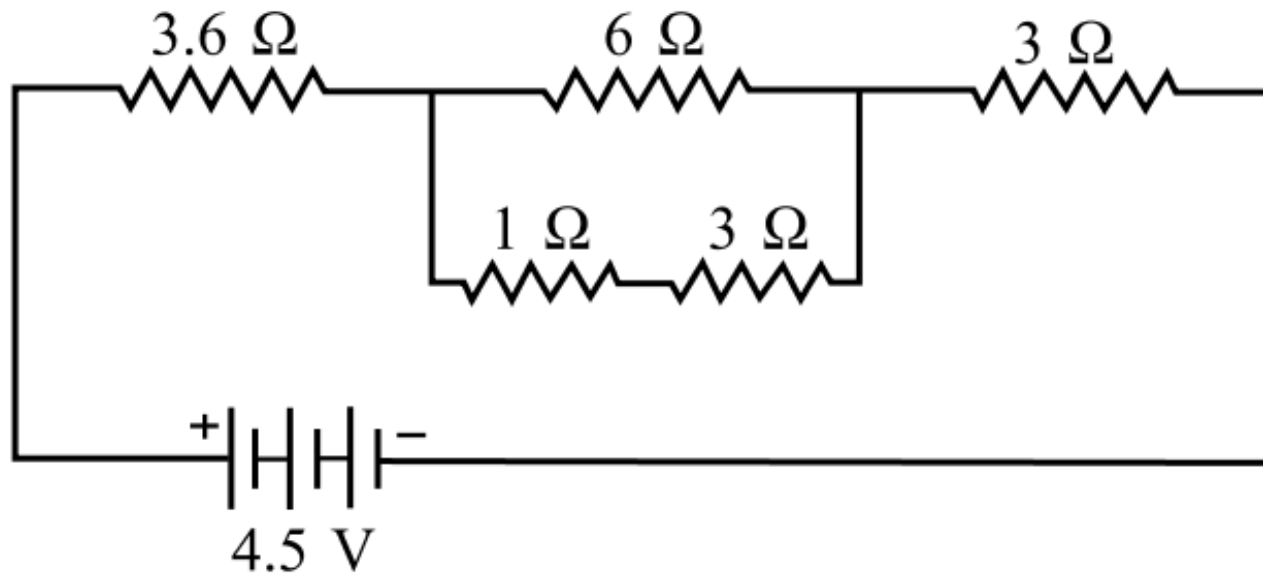


## CASE STUDY QUESTION 05

**Read the following and answer any four questions from (i) to (v)**

Shyam made one circuit for his Physics. He used five resistances: two  $3\Omega$ , one  $1\Omega$ , one  $6\Omega$ , one  $3.6\Omega$  and a battery of  $4.5\text{ V}$ . The circuit diagram is given below:



(i) Total resistance of parallel combination is :

- (a)  $2.4 \Omega$       (b)  $3 \Omega$       (c)  $6 \Omega$       (d)  $2 \Omega$

$1 \Omega$  and  $3 \Omega$  are in series.

$$\frac{1}{R} = \frac{1}{6} + \frac{1}{1+3} = \frac{1}{6} + \frac{1}{4} = \frac{5}{12}$$


$$\Rightarrow R = \frac{12}{5} = 2.4 \Omega$$

(ii) Equivalent resistance of total circuit is :

- (a)  $5 \Omega$       (b)  $9 \Omega$       (c)  $11 \Omega$       (d)  $13 \Omega$

$$R_1 = R + 3.6 + 3$$

$$= 2.4 + 3.6 + 3 = 9 \Omega$$

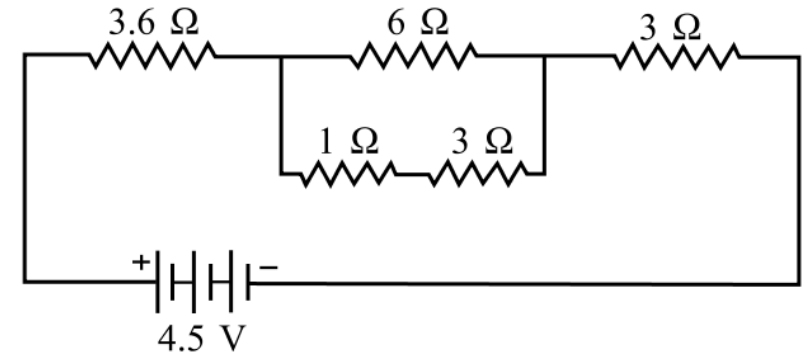

(iii) Total current in the circuit is :

- (a) 2 A            (b) 4.5 A            (c) 0.5 A            (d) 10 A


$$I = \frac{V}{R_1} = \frac{4.5 \text{ V}}{9 \Omega} = 0.5 \text{ A}$$

(iv) Current in 6 ohm resistance is

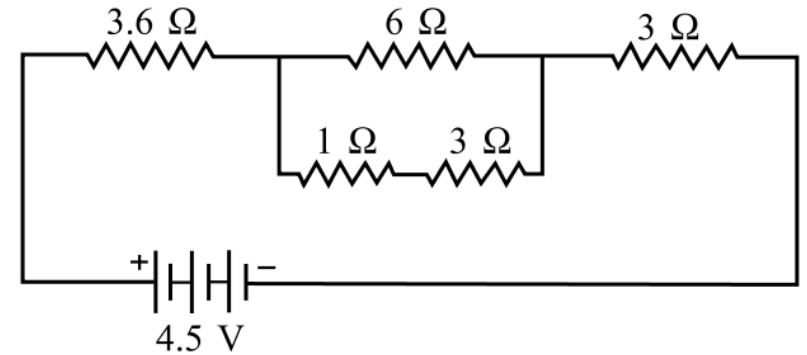- (a) 0.3 A            (b) 0.2 A            (c) 4 A            (d) 6 A

$$V = IR_l = 0.5 \times 2.4 = 1.2 \text{ V}$$

$$\therefore I_1 = \frac{1.2 \text{ V}}{6 \Omega} = 0.2 \text{ A}$$



(v) Potential across 3.6 ohm resistance will be :

- (a) 1.8 V      (b) 2.6 V      (c) 9 V      (d) 4.5V

$$\begin{aligned}V_I &= I \times 3.6 \Omega \\ &= 0.5 \text{ A} \times 3.6 \Omega \\ &= 1.8 \text{ V}\end{aligned}$$

