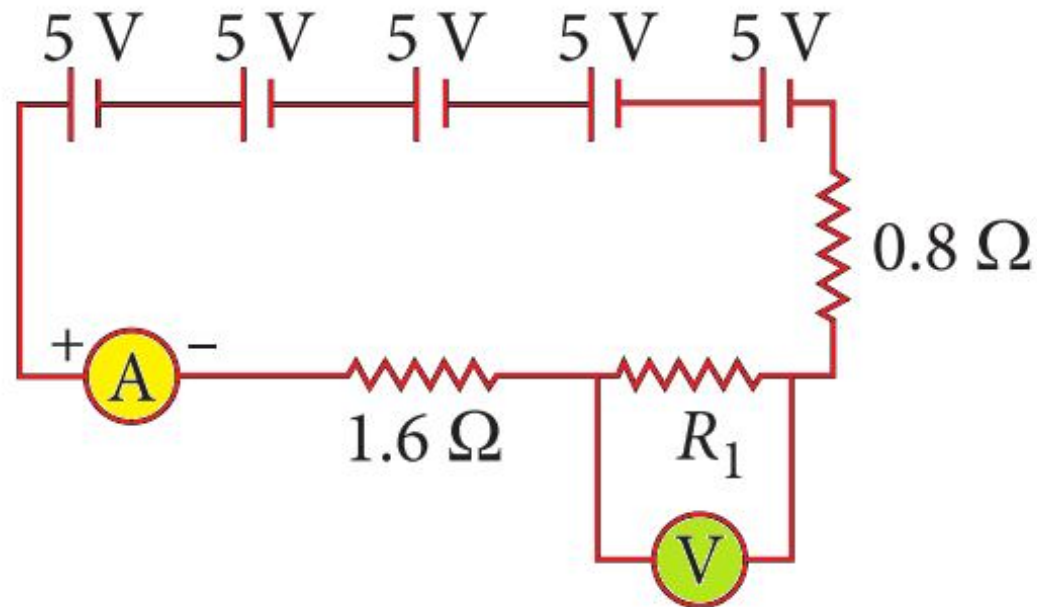


CASE STUDY QUESTION 19

Read the following and answer any four questions from (i) to (v)

Five cells each of emf 5 V are connected in series. The combination in series is joined to an ammeter of negligible resistance, a 1.6 W resistor, a 0.8 W resistor and an unknown resistor R_1 as shown in figure. The current in the circuit is 10 A. Assume the voltmeter to be ideal.



(i) Find the value of R_1 .

- (a) 2Ω (b) 0.1Ω (c) 0.5Ω (d) 5Ω

$$\text{Total emf} = 5 \text{ V} + 5 \text{ V} + 5 \text{ V} + 5 \text{ V} + 5 \text{ V} = 25 \text{ V}$$

$$\begin{aligned} \text{Total resistance of the circuit, } R &= 1.6 \Omega + 0.8 \Omega + R_1 \\ &= (2.4 + R_1) \Omega \end{aligned}$$


$$\text{Current in the circuit, } I = \frac{\text{Total emf}}{\text{Total resistance}} \quad \text{or } 10 = \frac{25}{2.4 + R_1}$$

$$\text{or } 24 + 10R_1 = 25 \quad \text{or } R_1 = 0.1 \Omega$$

(ii) The value of current across resistor R_1 is

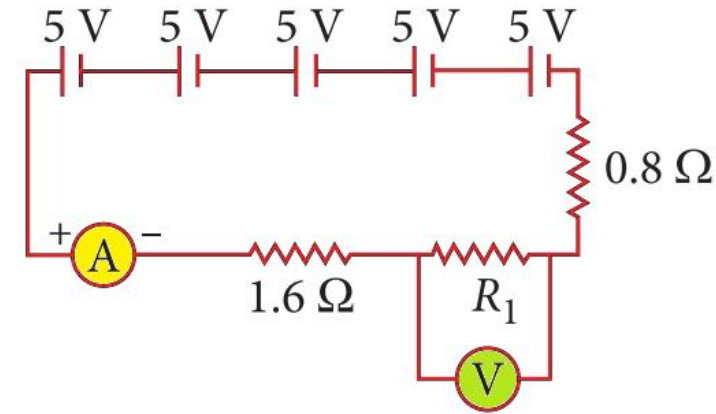- (a) 3 A (b) 0.5 A (c) 10 A (d) 2.5 A

As current flowing in the circuit is 10 A, so current through R_1 will also be 10 A.



(iii) Total resistance of the circuit is

- (a) 4Ω (b) 2Ω (c) 0.5Ω (d) 2.5Ω

$$\begin{aligned} \text{Total resistance of the circuit, } R &= 2.4 + 0.1 \\ &= 2.5 \Omega \end{aligned}$$

(iv) Find the value of potential difference across R_1 .

- (a) 1 V (b) 2 V (c) 3 V (d) 4 V

$$\begin{aligned} \text{Potential difference across } R_1, V &= I R \\ &= 10 \times 0.1 \\ &= 1 \text{ V} \end{aligned}$$

(v) If the voltmeter is not ideal, then current in the circuit will

- (a) increase (b) decrease (c) remain same (d) can't say.

If voltmeter is not ideal, then total resistance in the circuit decreases.

Hence, current through the circuit increases.

