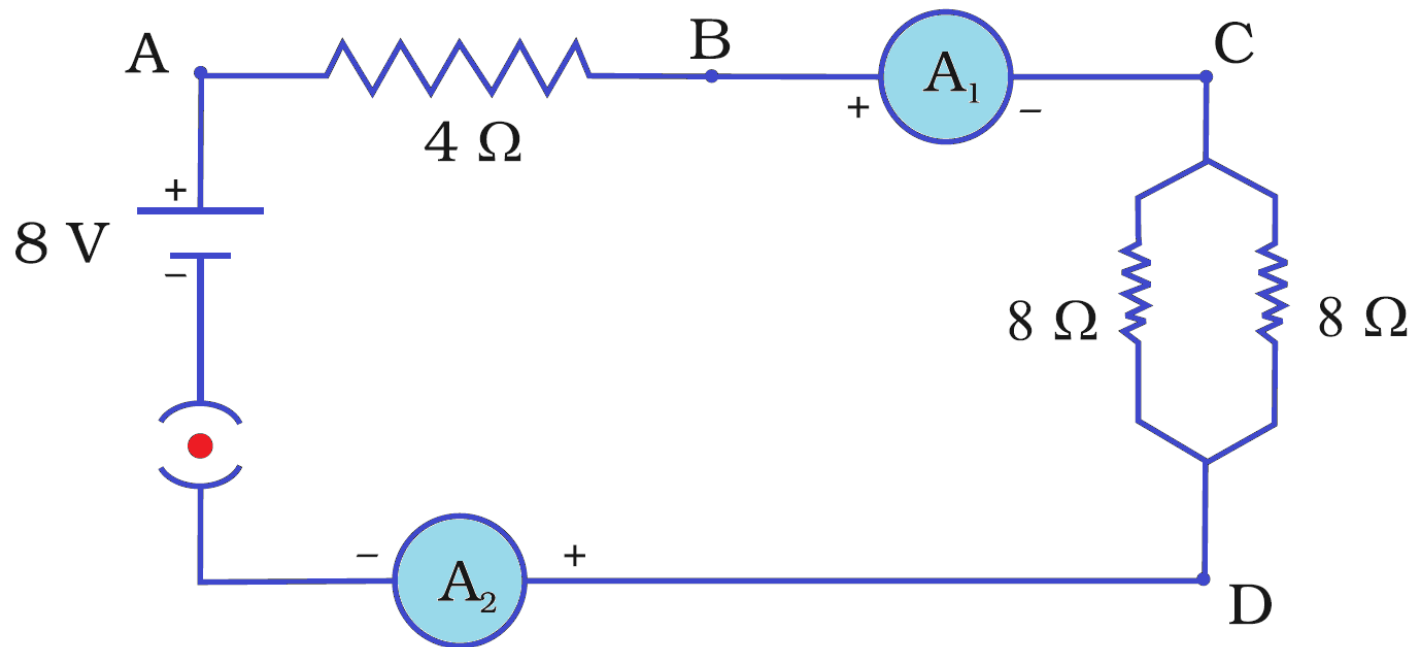


CASE STUDY QUESTION 37

Read the following and answer any four questions from (i) to (v)

Aditya decided to complete his Physics Project. He purchased three resistors $4\ \Omega$, $8\ \Omega$ and $8\ \Omega$ from the shop. Later he purchased a $8\ \text{V}$ battery, switch (which works as key) and two ammeters to complete his circuit as shown below:



(i) Find the effective resistance of two 8 resistors in the combination

- (a) 2Ω (b) 4Ω (c) 3Ω (d) 5Ω

$$R_p = \frac{8 \times 8}{8 + 8} = \frac{64}{16} = 4\Omega$$

(ii) Find the current flowing through the circuit.

- (a) 1.2 A (b) 1.5 A (c) 1 A (d) 2 A


$$V = IR$$

$$8 = I(4 + 4) \Rightarrow I = 1A$$

(iii) Find the potential difference across 4Ω resistance.

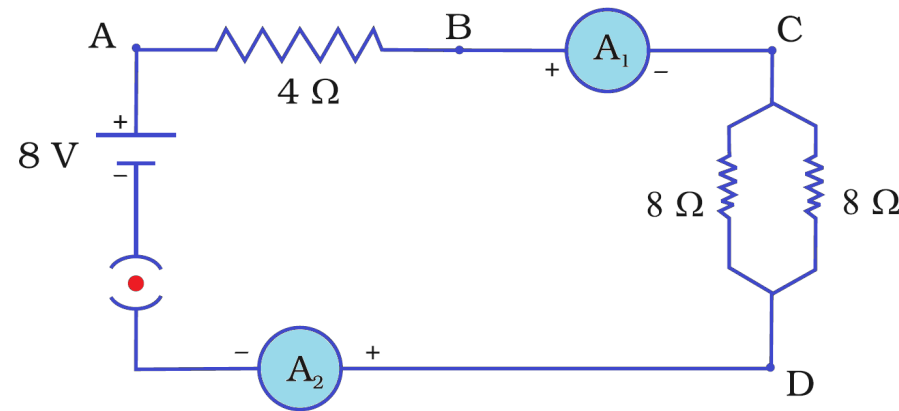- (a) 2 V (b) 3 V (c) 4 V (d) 5 V

$$\begin{aligned} \text{Potential difference across } 4\Omega \text{ resistor} &= IR \\ &= 1 \times 4 = 4 \text{ volt} \end{aligned}$$



(iv) Find the power dissipated in $4\ \Omega$ resistor

- (a) 2 W (b) 3 W (c) 4 W (d) 5 W

$$\begin{aligned}\text{Power dissipated in } 4\Omega \text{ resistor} &= I^2R \\ &= (1)^2 \times 4 \\ &= 4\text{W}\end{aligned}$$

(v) Find the difference in ammeter readings.

- (a) 1 (b) 2 (c) 3 (d) No difference

There will be no difference in ammeter readings as the ammeters are connected in series.

